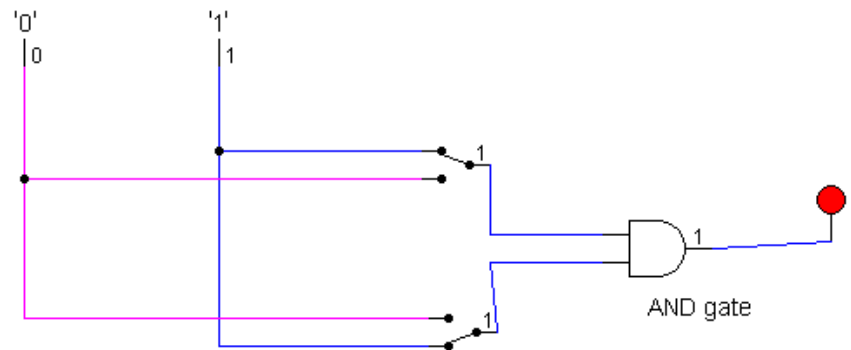


**Instruction:**Complete all questions in **1 hour**.

1. Draw the logic diagram of the following gates using logsim and complete the Truth tables.

a) AND


A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1



Prepared by: Karan Sunar

b) NOR (do the same as in Q No a for all of the following)


A	B	A+B	(A+B)'
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

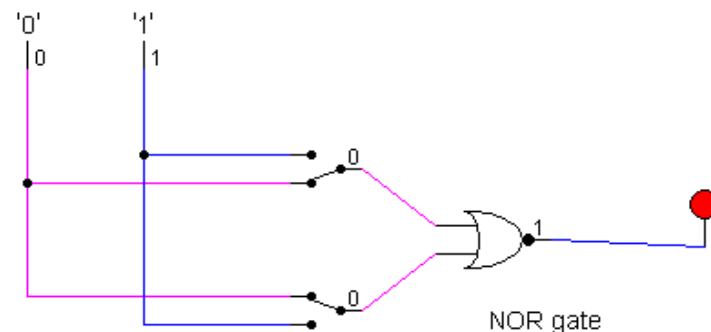

Prepared by: Karan Sunar

c) OR


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

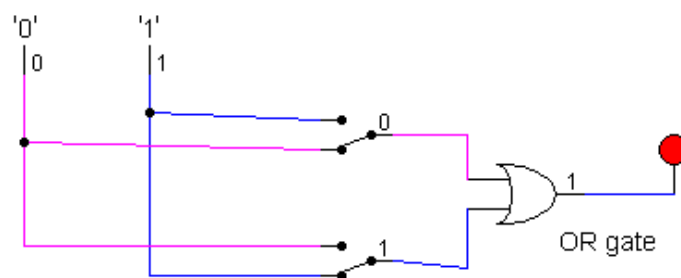

Prepared by: Karan Sunar

## d) NAND (using NOT and AND)


A	B	A.B	(A.B)'
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

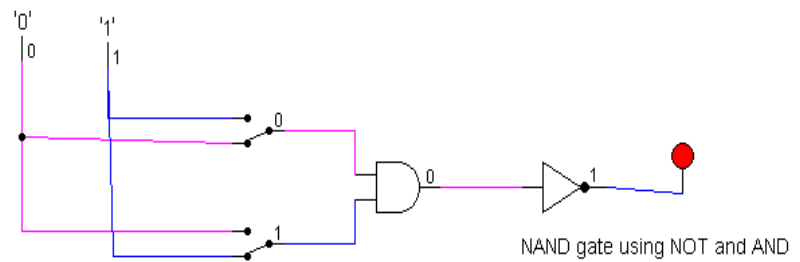

Prepared by: Karan Sunar

## e) XOR using AOI

A	B	A.B'	A'.B	A.B'+A'.B
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0


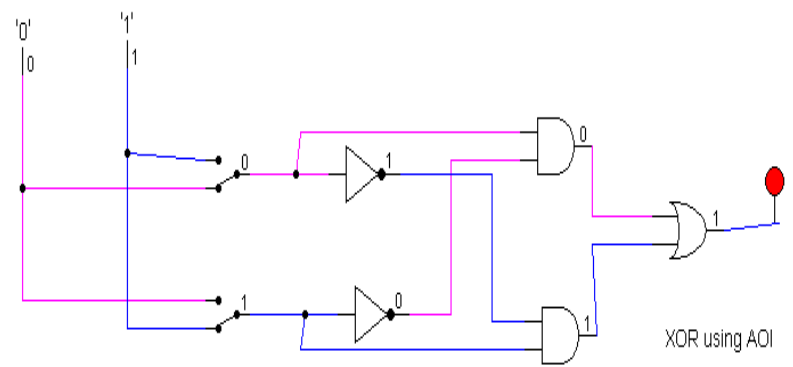


Prepared by: Karan Sunar

2. Use LogSim to build the equivalent circuit for the following Boolean equations.  
Prove that the expressions are equivalent by computing the truth table.



$$\neg(A + B) = \neg A \cdot \neg B$$

A	B	$\neg(A+B)$	$\neg A \cdot \neg B$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

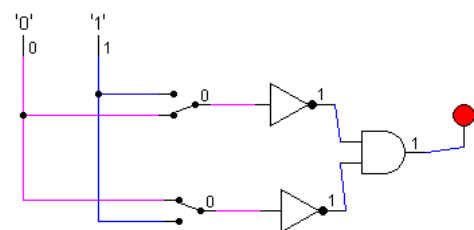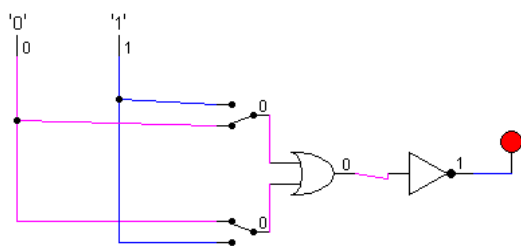

Prepared by: Karan Sunar

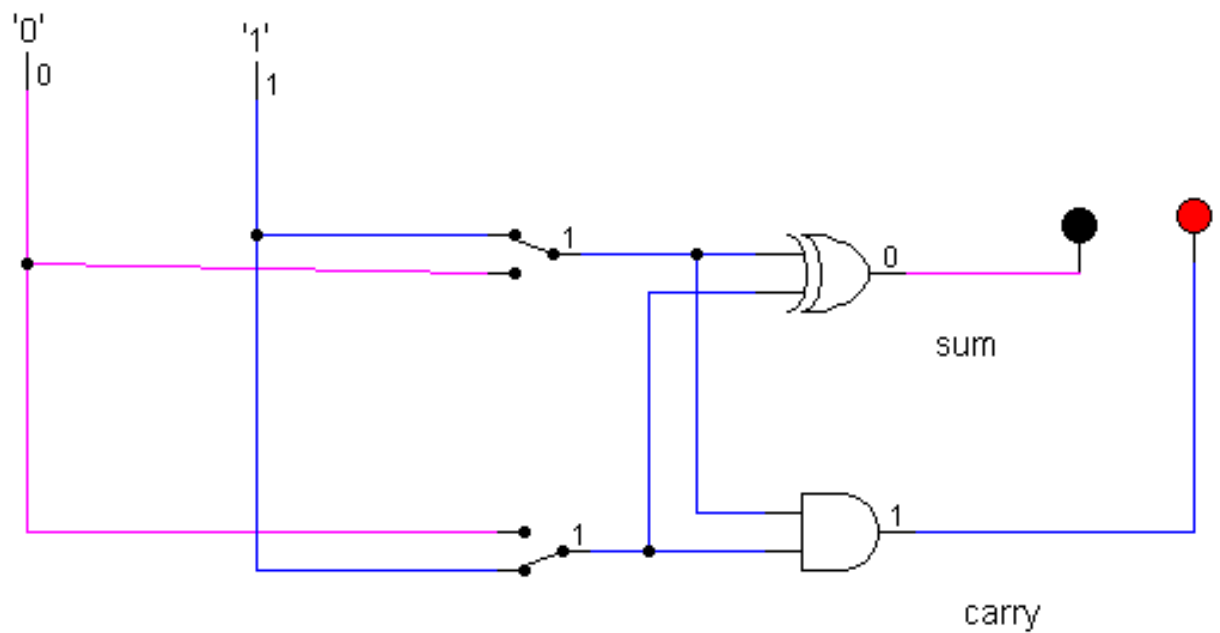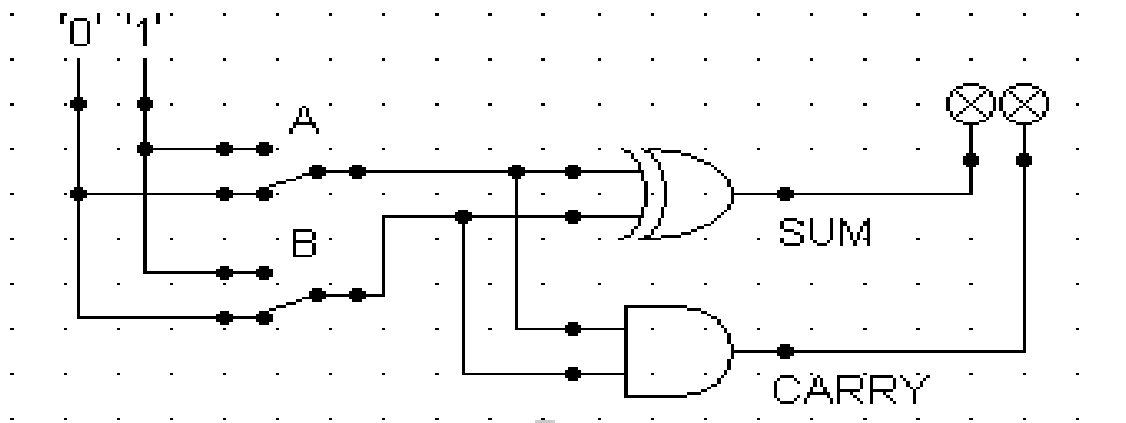
3. Draw the following circuit of half adder using LogSim



Prepared by: Karan Sunar


4. Draw full adder using Logsim and construct truth table.


A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

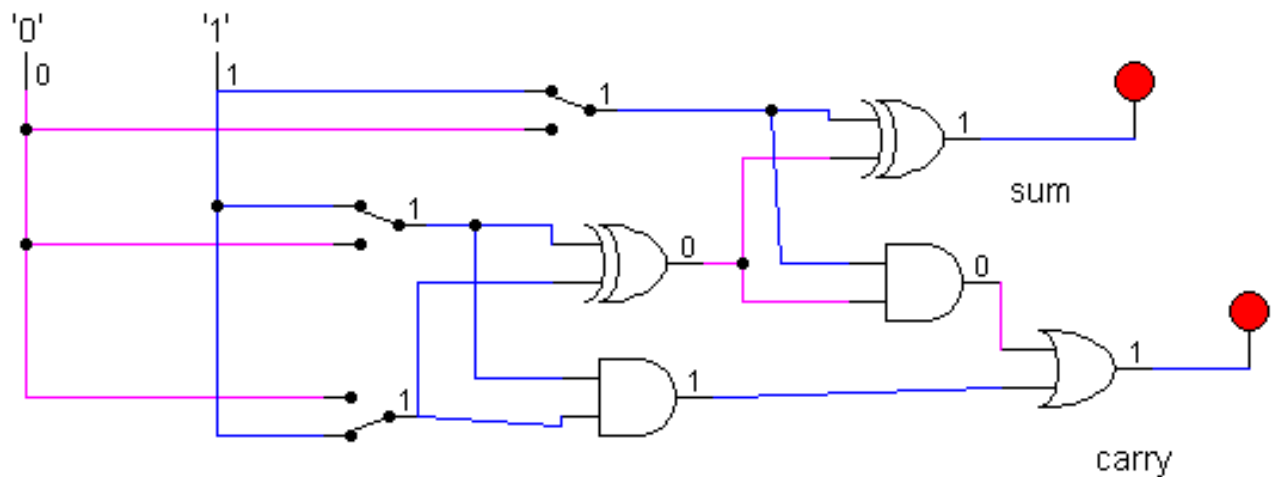


5. Draw the logic circuit for the following Boolean equations using logsim simulator.

a.  $AB+C$

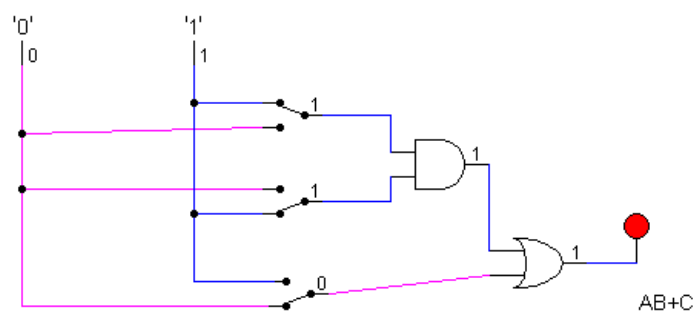

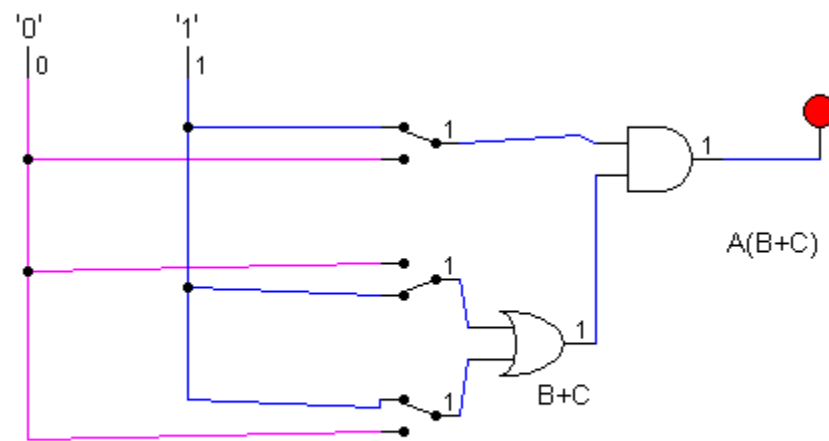b.  $A(B+C)$ 

Prepared by: Karan Sunar

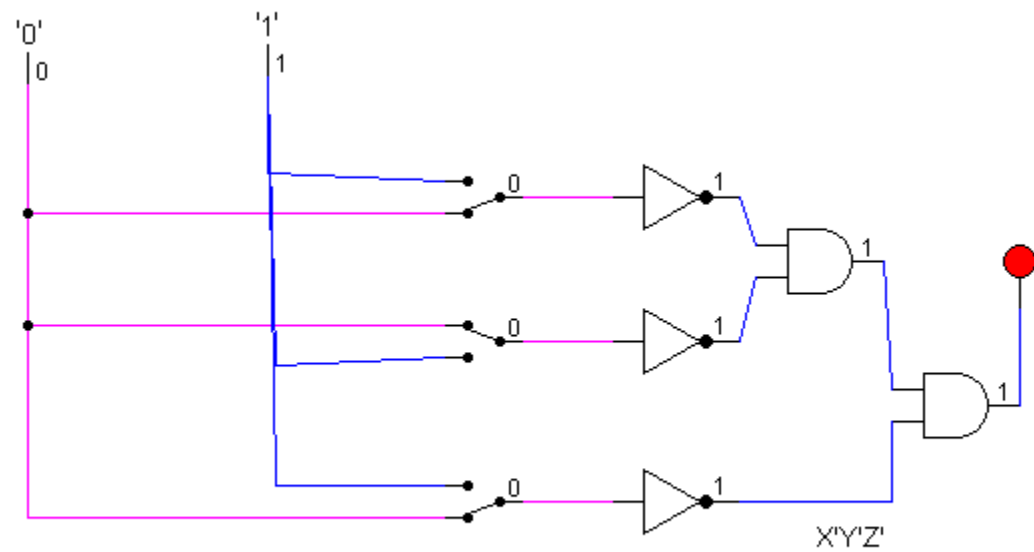c.  $X'Y'Z'$ 

Prepared by: Karan Sunar

.....THANK YOU .....